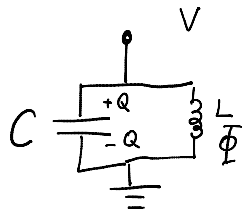


Lecture 5

Freitag, 21. Oktober 2011
09:34

parallel LC oscillating circuit:



Voltage across oscillator:

$$V = \frac{Q}{C} = - \frac{d\Phi}{dt} = -L \frac{dI}{dt}$$



energy stored in the circuit: (Hamiltonian)

$$H = \underbrace{\frac{1}{2} \cdot C V^2}_{\text{capacitive (electrostatic) energy}} + \underbrace{\frac{1}{2} L I^2}_{\text{inductive (magnetic) energy}} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} \frac{\Phi^2}{L}$$

Φ ... magnetic flux stored in the inductor
 Q ... charge stored on the capacitor

mechanical harmonic oscillator:
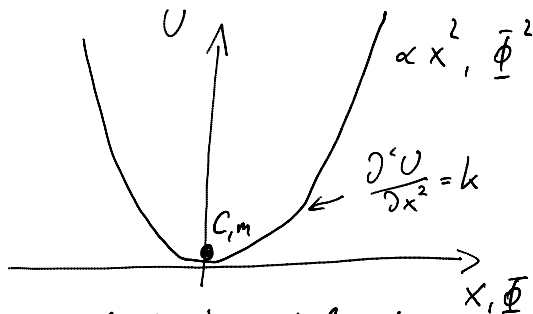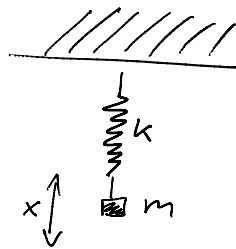
$$H = \underbrace{\frac{p^2}{2m}}_{\text{kinetic energy}} + \underbrace{\frac{k}{2} x^2}_{\text{potential energy}}$$



(virtual) particle of mass m (C) moving in potential

Characteristic quantities:

<u>mechanical</u>	<u>electronic</u>	HO
position x	flux Φ	} canonical conjugate variables
momentum p	charge Q	
mass m	capacitance C	
spring constant k	inverse inductance $\frac{1}{L}$	
frequency $\omega = \sqrt{\frac{k}{m}}$	$\omega = \frac{1}{\sqrt{LC}}$	

Quantum harmonic oscillator

$$x \rightarrow \hat{x} \qquad \Phi \rightarrow \hat{\Phi}$$

$$p \rightarrow \hat{p} = -i\hbar \frac{\partial}{\partial x} \qquad Q \rightarrow \hat{Q} = -i\hbar \frac{\partial}{\partial \Phi}$$

Commutation relations:

$$[\hat{x}, \hat{p}] = i\hbar \qquad [\hat{\Phi}, \hat{Q}] = i\hbar \quad \text{flux-charge } \left| \cdot \frac{1}{\hbar} \right.$$

$$\Leftrightarrow \left[2\pi \frac{\hat{\Phi}}{\Phi_0}, \frac{\hat{Q}}{2e} \right] = [\hat{J}, \hat{N}] = i \quad \text{phase-number}$$

Hamilton operator

$$H = \frac{\hat{Q}^2}{2C} + \frac{\hat{\Phi}^2}{2L} = -\frac{\hbar^2}{2C} \frac{\partial^2}{\partial \Phi^2} + \frac{1}{2L} \hat{\Phi}^2$$

Φ_0 ... magnetic flux quantum $\frac{h}{2e}$

creation and annihilation operators


$$\hat{a}^{\dagger} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q}^{\dagger} - i \hat{\Phi}^{\dagger}) \quad \text{creation operator}$$

$$\hat{a} = \frac{1}{\sqrt{2\hbar Z_c}} (Z_c \hat{Q} + i \hat{\Phi}) \quad \text{annihilation operator}$$

$$Z_c = \sqrt{\frac{L}{C}}, \quad \omega = \frac{1}{\sqrt{LC}} \quad \text{impedance, resonance freq.}$$

$$\Rightarrow \hat{H} = \hbar\omega \left(\hat{a}^{\dagger} \hat{a} + \frac{1}{2} \right) \quad \hat{a}^{\dagger} \hat{a} \dots \text{number operator}$$

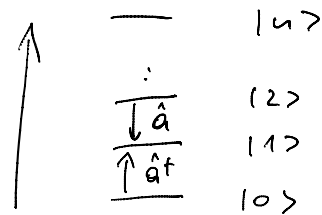energy level spectrum
equidistant level
spacing



properties

$$\hat{a}^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle$$

$$\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$$

$$\hat{a}^\dagger \hat{a} |n\rangle \equiv \hat{n} |n\rangle = n |n\rangle$$

$|n\rangle \dots$ Fock state with
 n excitations

relation to \hat{Q} , $\hat{\Phi}$ & \hat{V} , \hat{I} (inverse relations)

$$\hat{Q} = \sqrt{\frac{\hbar}{2Z_c}} (\hat{a}^\dagger + \hat{a}) \quad \hat{\Phi} = i \sqrt{\frac{\hbar Z_c}{2}} (\hat{a}^\dagger - \hat{a})$$

$$\text{or } \hat{V} = \frac{\dot{\hat{Q}}}{C} = \sqrt{\frac{\hbar C}{2C^2 L}} (\dot{\hat{a}}^\dagger + \dot{\hat{a}}) = \sqrt{\frac{\hbar \omega}{2C}} (\dot{\hat{a}}^\dagger + \dot{\hat{a}})$$


$$\hat{I} = \frac{\dot{\hat{\Phi}}}{L} = i \sqrt{\frac{\hbar \omega}{2L}} (\dot{\hat{a}}^\dagger - \dot{\hat{a}}) \quad [\omega = \frac{1}{LC}]$$

Josephson junction as Non-linear Inductor:

induction law: $V = -L \dot{I}$

Josephson relation: $I = I_0 \cdot \sin \varphi$

(supercurrent across
junction)

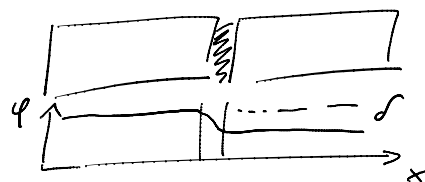

$$V = \frac{\Phi_0}{2\pi} \dot{\varphi} \quad [ac]$$

(time-dependent phase
if voltage is applied)

$$\dot{I} = I_0 \cdot \cos \delta \dot{\delta} \Rightarrow \boxed{V = \frac{\Phi_0}{2\pi I_0} \frac{1}{\cos \delta} \dot{I} \equiv L_J \dot{I}}$$

Josephson Inductance: $L_J = L_{J0} \left(\frac{1}{\cos \delta} \right) \rightarrow$ non-linearity

$$L_{J0} = \frac{\Phi_0}{2\pi I_0} \text{ specific Josephson inductance}$$

Josephson Energy: $E_J = \int V I dt'$

$$= \int \frac{\Phi_0 I_0}{2\pi} \dot{\delta} \sin \delta dt$$

$$= \int \frac{\Phi_0 I_0}{2\pi} \sin \delta d\delta = \frac{\Phi_0 I_0}{2\pi} \cos \delta$$


$$\boxed{= E_{J0} \cos \delta \text{ with } E_{J0} = \frac{\Phi_0 I_0}{2\pi}}$$

Typical parameters: $I_0 = 100 \text{ nA}$

$$\Rightarrow L_{J0} = \frac{\Phi_0}{2\pi I_0} \approx 3 \text{ nH} \quad (\sim 3 \text{ mm of wire})$$

$$\Rightarrow E_{J0} = \frac{\Phi_0 I_0}{2\pi} \approx 50 \text{ GHz}$$

Dissipation:

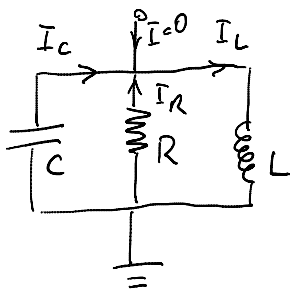

$$I_c + I_R = I_L \quad (\text{Kirchhoff-Law})$$

- current through resistor: $I_R = \frac{V}{R}$

- displacement current:

$$I_c = \dot{Q}_c = C \dot{V}$$

- voltage across inductor

$$V = -L \dot{I}_L$$

$$\Rightarrow -C\dot{V} - \frac{V}{R} + \dot{I}_L = 0$$

same voltage across elements:

$$\Rightarrow CL\ddot{I}_L + \frac{L}{R}\dot{I}_L - I_L = 0$$

$$\Rightarrow \left[\ddot{I}_L + \frac{1}{RC}\dot{I}_L - \frac{1}{LC}I_L = 0 \right]$$

Differential equation for current through inductor

Solution: $I_L(t) = I_L(0)e^{\lambda t}$ $\lambda_{1,2} = \frac{1}{2LC} \left(-\frac{L}{R} \pm \sqrt{\left(\frac{L}{R}\right)^2 - 4LC} \right)$

($4LC \gg \frac{L}{R}$... underdamped oscillator)

$$\lambda_{1,2} = -\frac{1}{2RC} \pm i\sqrt{\frac{1}{LC}} = -\frac{\alpha}{2} \pm i\omega$$


$$\alpha = \frac{1}{RC} \equiv \frac{1}{\tau} \quad \text{decay constant}$$

$$\tau = RC \quad \text{decay time}$$


$$\omega = \frac{1}{\sqrt{LC}} \quad \text{angular frequency}$$

Energy decay rate:
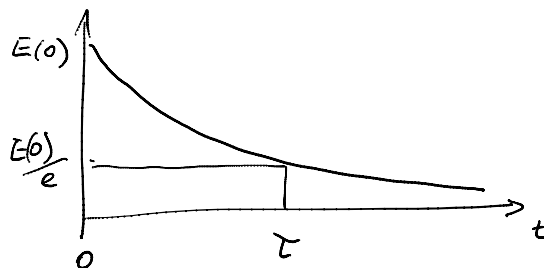
$$E \propto L\dot{I}_L^2 \propto e^{-\frac{1}{RC}t} = e^{-\frac{t}{\tau}}$$



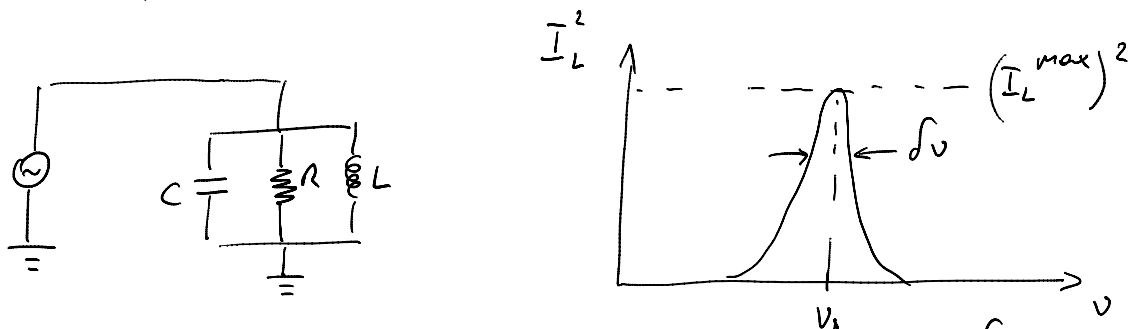spectral response: (driven damped oscillator)



Lorentzian line shape: $I_L^2(\nu) = \frac{(\bar{I}_L^{\max})^2}{(\nu - \nu_0)^2 + \frac{\delta \nu^2}{4}}$


$\delta \nu = \frac{1}{2\pi\tau}$... full width at half maximum

Quality factor: $2\pi \frac{\text{Energy stored}}{\text{Energy lost per cycle}} \hat{=} \frac{\nu_0}{\delta \nu}$

$= 2\pi \nu_0 \cdot \tau = \omega_0 \cdot R \cdot C$

in QM: excited state decay rate. $\Gamma_1 = \frac{1}{\tau} = \frac{1}{RC}$

Internal & external dissipation:

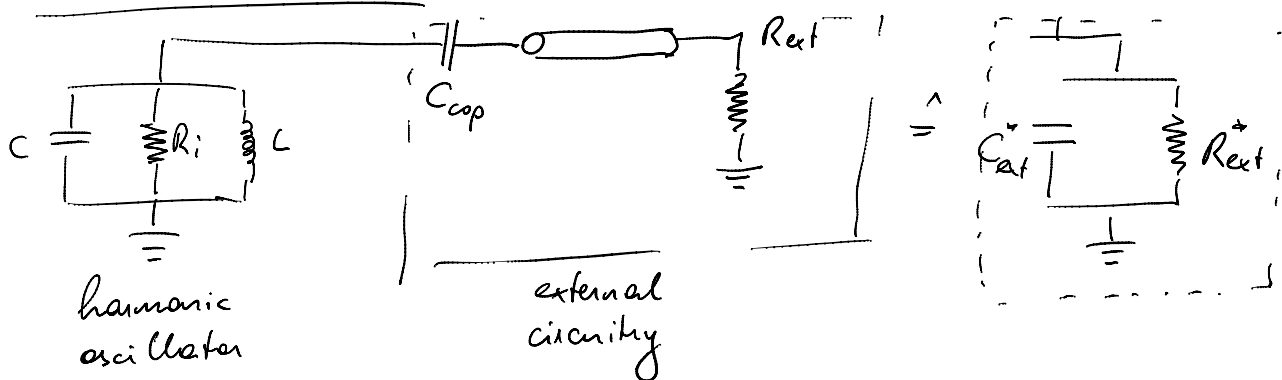

• total effective resistance (parallel capacitance) $\frac{1}{R_{\text{tot}}} = \frac{1}{R_{\text{int}}} + \frac{1}{R_{\text{ext}}} \rightarrow$ external contribution to energy decay

capacitance $C_{\text{tot}} = C_{\text{int}} + C_{\text{ext}}$

energy decay time $\tau = R_{\text{tot}} C_{\text{tot}}$